

Circuit and Systems

Date _____

Page _____

Assignment - 4

Name - Syeda Reeha Ansar

Roll no. - 14114802719

Ans 1. Necessary and sufficient conditions for any rational function to be the real func :-

- 1) Both $A(s)$ and $B(s)$ polynomials in $f(s) = \frac{A(s)}{B(s)}$ if $B(s)$ are unity so poles and zeroes of PR func \Rightarrow cannot have real points i.e. they can't be in right half of S-plane
- 2) Highest and lowest powers of $A(s)$ and $B(s)$ differ by unity
- 3) If $P(s)$ is a PR func \Rightarrow , then reciprocal of $F(s)$ is also a PR func \Rightarrow .
- 4) The sum of PR func \Rightarrow is also a PR func \Rightarrow but diff of two PR func \Rightarrow is not necessarily a PR func

Ans 2. Properties of LC, RC and RL network func \Rightarrow

- (i) $Z_{LC}(s)$ and hence $\gamma_{LC}(s)$ are the ratio of even to odd to even polynomials. (This property is also called as " Foster Resistance Theorem" since both $M_i(s)$ and $N_j(s)$ are unity they have only imaginary roots and it follows that the poles and zeroes of $Z_{LC}(s)$ on γ_{LC} are on the imaginary axis (including origin))

3. The poles and zeroes interlace (or alternate) on jw axis
4. The highest power of Numerator and denominator must differ by unity.
5. The lowest power of Numerator and denominator must also differ by unity.
6. There must be zero or a pole at origin and infinity.

Properties of R-L admittance func" or R-C impedance

1. The poles and zeroes lie on -ve real axis (including origin) of the complex s-plane
2. The poles and zero interlace (or alternate) along the -ve real axis
3. The residues of poles of $Z_{R-C}(s)$ or $Y_{R-L}(s)$ must be real and +ve.
The residues of $Y_{R-C}(s)$ or $Z_{R-L}(s)$ are real and -ve
4. The singularity nearest to (or at) origin must be a pole i.e. func " Z_{R-C} or Y_{R-L} $\rightarrow \infty$ with $s \rightarrow 0$
5. The singularity nearest to (or at) the origin must be a pole i.e. func " Z_{R-C} or $Y_{R-L} \rightarrow 0$ and $s \rightarrow \infty$

Properties of R-L impedances or R-C admittances

1. The poles and zeroes lie on -ve real axis (including origin) of the complex s-plane
2. The poles and zeroes intersect along -ve real axis
3. a) The residue of poles of $Z_{R-L}(s)$ or $Y_{R-C}(s)$ are real or -ve
b) Residue at poles $Y_{R-L}(s)$ or $Z_{R-L}(s)$ must be real and +ve.
4. The singularity nearest to (or at) the minus $(-\infty)$ must be a pole zero i.e. finite $Z_{R-L}(s)$ or $Y_{R-C}(s) \rightarrow 0$ with $s \rightarrow 0$
5. The singularity nearest to (or at) the origin must be $(+\infty)$ must be a pole i.e. finite $Z_{R-L}(s)$ or $Y_{R-C}(s) \rightarrow \infty$ with $s \rightarrow \infty$.

Ans 3. a) $\frac{Z(s)}{I(s)} = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$

$$N(s) = s^3 + 7s \quad M(s) = 4s^2 + 9$$

$$4s^2 + 9 \quad | \quad s^3 + 7s \quad | \quad s/4$$

$$\left(\rightarrow \underline{s^3 + 7s/4} \right)$$

$$19/4 \quad | \quad 4s^2 + 9 \quad | \quad 16s/19$$

$$F(s) = M_1 M_2 - N_1 N_2$$

$$Is = \beta w \geq 0$$

$$\begin{aligned} & \rightarrow \frac{4s^2}{9} \\ & | \quad 19/4s \quad | \quad 19/35 \\ & \approx 19s/4 \\ & \underline{x} \end{aligned}$$

$$\begin{aligned}
 M_1(s) &= 5s^2 + 3 & N_1(s) &= s^3 + 9s \\
 M_2(s) &= 4s^2 + 9 & N_2(s) &= s^3 + 7s \\
 F(s) &= (5s^2 + 3)(4s^2 + 9) - (s^3 + 9s)(s^3 + 7s) \\
 &= -s^6 + 4s^4 - (s^2 + 27) & \text{if } s \in j\omega \\
 &= -(j\omega)^6 + 4(j\omega)^4 - 6(j\omega)^2 \omega^2 & \omega \geq 0 \\
 &= \omega^6 + 4\omega^4 + 6\omega^2 + 27 \geq 0
 \end{aligned}$$

Since given $f(s)$ is PR

Ans 6) $f(s) = \frac{s^2 + s + 1}{s^2 + s + 4}$ $M_1, M_2 - N_1, N_2 \geq 0$

$$\begin{aligned}
 M_1 &= s^2 + 1 & N_1 &= s \\
 M_2 &= s^2 + 4 & N_2 &= s \\
 (s^2 + 1)(s^2 + 4) - s^2 &\geq 0 \\
 s^4 + 5s^2 + 4 - s^2 &\geq 0 \\
 s^4 + 4s^2 + 4 &\geq 0 \quad |_{j\omega} > 0 \\
 (j\omega)^4 + 4(j\omega)^2 + 4 &\geq 0 \\
 \omega^4 + 4\omega^2 + 4 &\geq 0
 \end{aligned}$$

For any value ω it will remain +ve
So it is a PR funcⁿ

(i) $\frac{s^2 + 10s + 4}{s+2} = f(s)$

$$\begin{aligned}
 M_1, M_2 - N_1, N_2 &\geq 0 \\
 M_1 &= s^2 + 9 & N_1 &= 10s \\
 M_2 &= s+2 & N_2 &= s
 \end{aligned}$$

$$(s^2 + 4)_2 - 10s^2 \geq 0$$

$$2s^2 - 8 - 10s^2 \geq 0$$

$$-8s^2 + 8 \mid_{\text{in}} \geq 0$$

$$-8(jw)^2 + 8 \geq 0$$

$$8w^2 + 8 \geq 0$$

for every value of w it will remain true
so it is a pd func.

Ans 4 Foster - I Form

$$Z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)} \quad [Y_s = c]$$

$$= \frac{s^3 + 4s}{2s^4 + 20s^2 + 18}$$

using Partial fraction expression.

$$\frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)} = \frac{1}{2} \left[\frac{As + B}{s^2 + 1} + \frac{(8+1)}{(s^2 + 9)} \right]$$


$$A = 3/8, B = 0, D = 0, C = 5/8$$

$$\therefore = \left[\frac{3s/16}{s^2 + 1} + \frac{5s/16}{s^2 + 9} \right]$$

$$L_0 = 0, C_0 = 0 \quad C_1 = 16/3, \quad L_2 = 16/5$$

$$D_1 = 3/12, \quad D_2 = 5/144$$
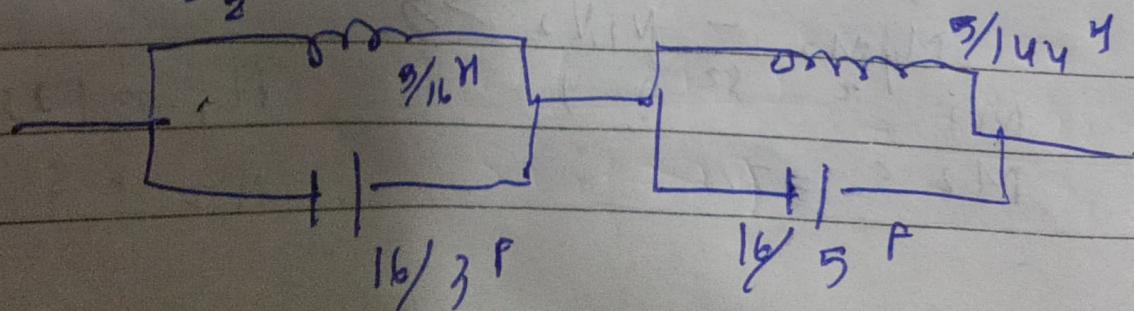
$$a < \frac{1}{L_2^{26/5}}, \quad L_2 = \frac{5}{144}$$



Form-II (LC network)

$$\text{Step I} \rightarrow V(s) = \frac{1}{Z(s)} e^{-\sqrt{(s^2+1)(s^2+9)}} \\ = \frac{2s^4 + 20s^2 + 18}{s^3 + 4s} \quad \text{LC} \Rightarrow N/D$$

$$\frac{s^4}{s^3} \approx s$$

$$\text{Step II} \rightarrow N > D \quad s^3 + 4s \left[2s^4 - 2s^2 + 18 \right] \cancel{+ 2s^2} \quad [2s]$$

$$\begin{array}{r} 2s^4 \\ - 2s^2 \\ \hline \end{array}$$

$$V = Q + R/D = \frac{2s + 12s^2 + 18}{s^3 + 4s} \quad 12s^2 + 18$$

Step III using partial fraction: $V(s)$

$$\frac{12s^2 + 18}{s(s^2 + 4)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 4}$$

$$A = 9/2 \quad \& \quad C = 0, \text{ and } B = 15/2$$

$$V(s) = \frac{2s + 9/2}{s} + \frac{15/2}{s^2 + 4}$$

$$\text{Step IV} \quad \frac{1}{L_1 s} + \frac{6s + \frac{9}{2}}{(1/L_1 + s^2)} + \frac{s/2}{(1/L_2 + s^2)} + \dots$$

$$V(s) = 2s + \frac{9/2}{s} + \frac{15/2}{s^2 + 4}$$


$$V(s) = 2s + \frac{1}{(1/L_1)s} + \frac{s/(2/L_2)}{s^2 + 4} \quad \Rightarrow$$

$$L_1 C_1 = \frac{1}{4} \quad \& \quad \frac{1}{4L_2} = 4$$

$$\frac{1}{4} = 4L_1$$

$$\frac{1}{c_1} \approx \frac{8}{18}$$

$$C_1 = \frac{15}{8}$$

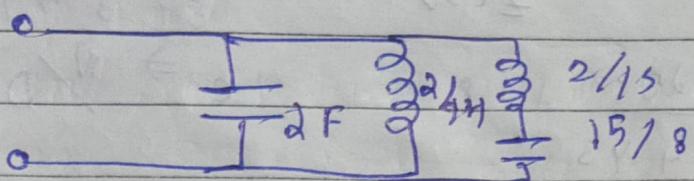

Why 5.

$$Z(s) = \frac{25412s^3 + 16s}{s^4 + 4s^2 + 3}$$

cancer - I form

$\frac{55}{54} = 50$, so 2 will come first


$$s^4 + s^2 + 3 \quad | \quad ds^5 + 12s^3 + 16s \quad 2s$$

$$2s^5 + 8s^3 + b_3$$

(-), (-), (-)

$$L_1 = 2, \quad C_1 = 1/4, \quad L_2 = 8/3$$

$$C_2 = 3/4, L_2 = 2/3$$

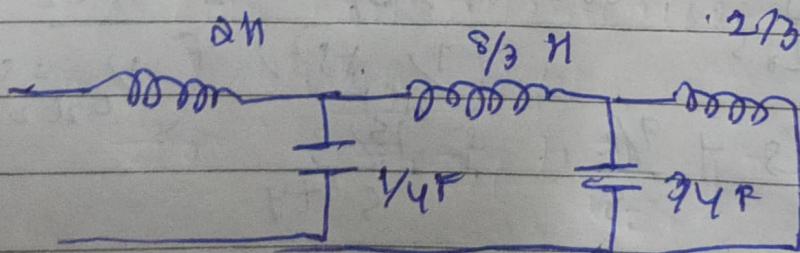

$$\text{Ans 6. } z(s) = \frac{(s^2+1)(s^2+3)}{s(s^2+2)} = \frac{s^4 + 3s^2 + s^2 + 3}{s^3 + 2s}$$

$$\frac{S^4 + 4S^2 + 3}{S^3 + 2S}$$


Cause - II form

LC, $\frac{S^4}{S^3} = S \rightarrow L$ will be first element

$$\begin{aligned} & 2S + S^3 \left[3 + 4S^2 + S^4 \right] \quad 3/S \text{ S} \\ & \underline{\underline{2S + \frac{3}{2}S^2}} \\ & \underline{\underline{S^2 + S^2 + S^4}} \quad 2S + S^3 \quad [4S \text{ S}] \\ & \underline{\underline{2S + \frac{4}{3}S^3}} \\ & \underline{\underline{S^2 + S^2 + S^4}} \quad \frac{2}{5}S \quad \left[\frac{2}{5}S \right] \\ & \underline{\underline{S^2 + S^2 + S^4}} \quad S^2 \quad \underline{\underline{S^2}} \end{aligned}$$

$$L_1 = 2/3, C_2 = 5/4,$$

$$L_2 = 2/15, C_3 = 5$$

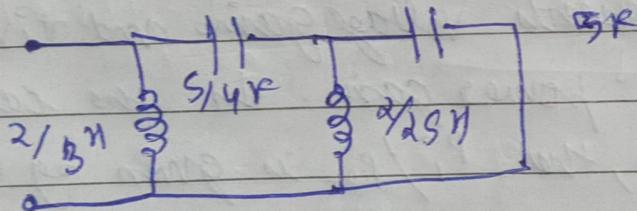

$$\begin{aligned} & S^4 \left[\frac{1}{5}S^3 \right] \text{ S} \\ & \underline{\underline{S^2}} \\ & X \end{aligned}$$

Ques. Parameters of a filter

→ Character impedance Z_c/Z_0

The character impedance of a filter must be chosen such that the filter may fit into a given line or b/w two types of equipments

→ Pass band

Band in which ideal filter have no attenuate pass all frequencies without reducing in mag.

are referred to as pass band

→ Stop band:

Band, in which ideal filter shows alternate freq. are referred to as stop frequencies

→ Unit of attenuation

The attenuation of a wave filter can be expressed in decibels (dB) or Neper or Beta.

Let V_i , I_i , and P_i be the input current and input power respectively of a filter. Similarly V_o , I_o and P_o represent output voltage, current and power.

The V_o/V_i represents voltage gain and P_o/P_i represents power gain. In the case of filter $P_o < P_i$ so, that P_i/P_o is given by attenuation

(Ans) a) Low Pass Attenuation

for -T network filter,

$$Z_{0T} = \sqrt{Z_1 Z_2 \left(\frac{L Z_L}{4 Z_2} \right)} = \sqrt{\frac{1}{C} \left(1 - \omega^2 C^2 \right)}$$

$$Z_{0T} = \sqrt{\frac{L}{C}} \sqrt{1 - \left(\frac{f}{f_0} \right)^2} = \frac{R_o}{\sqrt{1 - \left(\frac{f}{f_0} \right)^2}}$$

In the pass band, $f < f_c$, Z_{0T} is real

In stop band $f > f_c$, Z_{OT} is imaginary
and if $f = f_c$, $Z_{OT} = 0$


for π network filter,

$$Z_{OT} = \sqrt{\frac{Z_1 Z_2}{1 + \omega^2 L_1 C_2}} = \sqrt{\frac{L_1 C_2}{1 - \omega^2 L_1 C_2}} = \sqrt{\frac{L_1 C_2}{1 - (\omega/f_c)^2}}$$


In pass-band $f < f_c \Rightarrow Z_{OT}$ is real

In stop-band if $f > f_c$, Z_{OT} is imaginary
and if $f = f_c \Rightarrow Z_{OT} = 0$

If scan verified by $Z_{OT} = R_o$

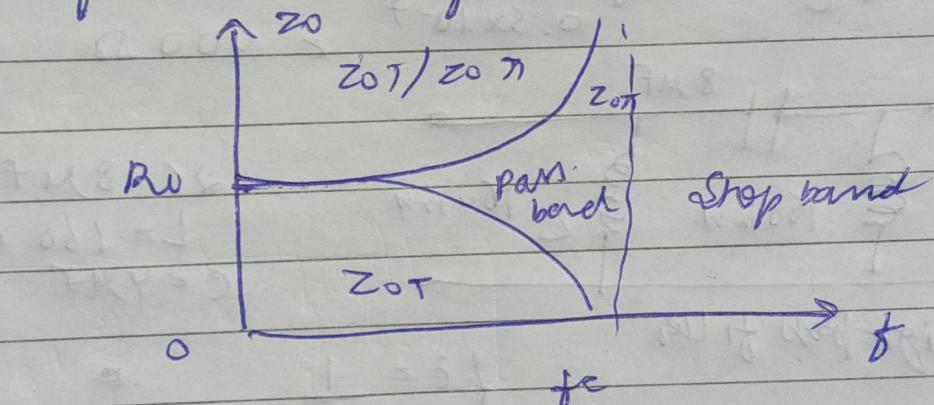

b) Constants and band pass filter

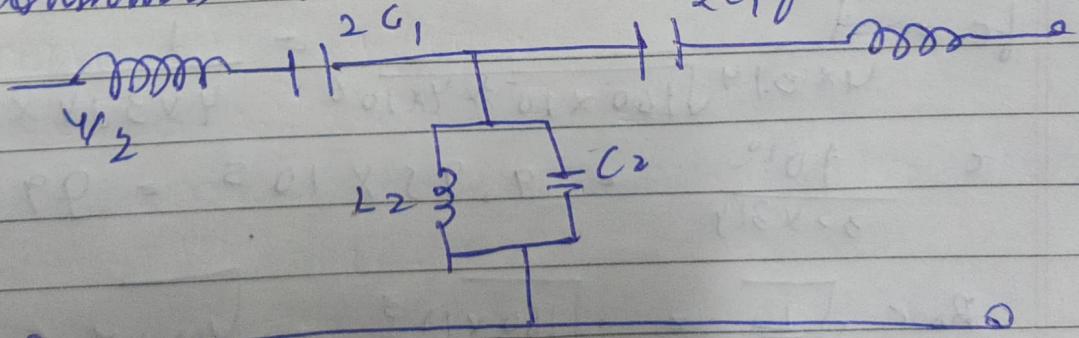


for series arm $\frac{Z_1}{2} = j \frac{\omega L_1}{2} + \frac{1}{j \omega C_1}$

$$\Rightarrow Z_1 = j \omega L_1 + \frac{1}{j \omega C_1} = j \left(\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right)$$

$$\hat{Z}_1 Z_2 = L_2 \frac{\left(1 - \omega^2 L_1 C_1\right)}{\left(1 - \omega^2 L_2 C_2\right)}$$

Ans 9. a)

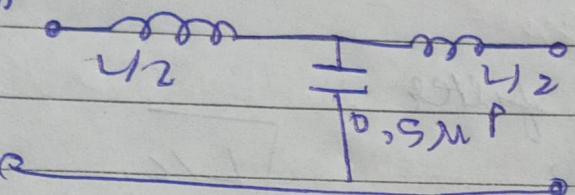


Low pass filter
 $\omega C = \sqrt{Y_L C}$

$$c = \sqrt{\frac{Y}{\omega/2 \times 2 \times 10^{-3} \times 0.5 \times 10^{-7}}} = \sqrt{\frac{4}{400 \times 10^{-10}}}$$

$$\sqrt{10^8} = 10^4 = 10 \text{ kHz}$$
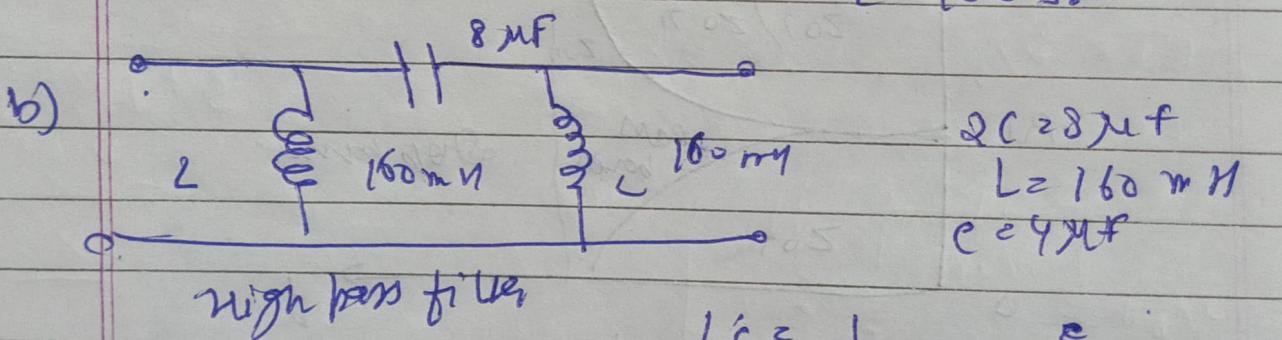
$$R_o = \sqrt{\frac{L}{C}} = \sqrt{\frac{8 \text{ mH} \times 10^{-3}}{0.5 \times 10^{-7}}} = \sqrt{6 \times 10^4} = 4 \times 10^2 = 400 \Omega$$



high pass filter

$$f_c = \frac{1}{4\pi \sqrt{LC}}$$

$$f_c = \frac{1}{4 \times 3.14 \sqrt{160 \times 10^{-3} \times 8 \times 10^{-6}}} = \frac{1}{4 \times 3.14 \times 8 \sqrt{10^{-8}}}$$

$$= \frac{10^1}{32 \times 314} = 9.95 \times 10^5 = 995 \text{ kHz}$$

$$R_o = \sqrt{\frac{L}{C}} = \sqrt{\frac{160 \times 10^{-3}}{4 \times 10^{-6}}} = \sqrt{4 \times 10^4} = 200 \Omega$$

Ans 1.

$$R_o = 600 \Omega$$

$$f_{c1} = 2 \text{ kHz}$$

$$f_{c2} = 5 \text{ kHz}$$

$$L_1 = \frac{R_o}{\pi (f_{c2} - f_{c1})} = \frac{600}{3.14 (5-2) \times 10^3} = 63.69 \text{ mN}$$

$$C_2 = \frac{f_{c2} - f_{c1}}{4\pi R_o f_{c1} f_{c2}} = \frac{(5-3) \times 10^3}{4 \times 3.14 \times 600 \times 2 \times 5 \times 10^3} = 0.02 \text{ MP}$$

$$L_2 = \frac{(f_{c2} - f_{c1}) R_o}{4\pi f_{c1} f_{c2}} = \frac{3 \times 10^3 \times 600}{4 \times 3.14 \times 5 \times 10^3} = 14.3 \text{ mN}$$

$$C_1 = \frac{1}{\pi k_o (f_{c2} - f_{c1})} = \frac{1}{3.14 \times 600 (3) \times 10^3} = 0.00017 \text{ MP}$$

Hence $\frac{L_1}{2} = 31.84 \text{ mN}$

