

Circuit and Systems

Assignment No. 4

Que-1 Write the necessary and sufficient conditions for any rational function to be positive real function.

Que-2 Write the properties of LC, RC & RL network functions.

Que-3 Check whether the given functions are positive real functions or not -

(i) $F(s) = \frac{s^2 + s + 1}{s^2 + s + 4}$

(ii) $F(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$

(iii) $\frac{s^2 + 10s + 4}{s + 2}$

Que-4 Synthesize the network function,

$$Z(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$$

as a Foster-I and Foster-II form.

Que-5 Synthesize the fⁿ $Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$

as Cauer-I form.


Que-6 Synthesize the fⁿ $Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$ as

Cauer-II form


Que-7 Define all parameters of a filter.

Que-8 Derive all characteristics of constant K
(a) low pass, (b) band pass filters.

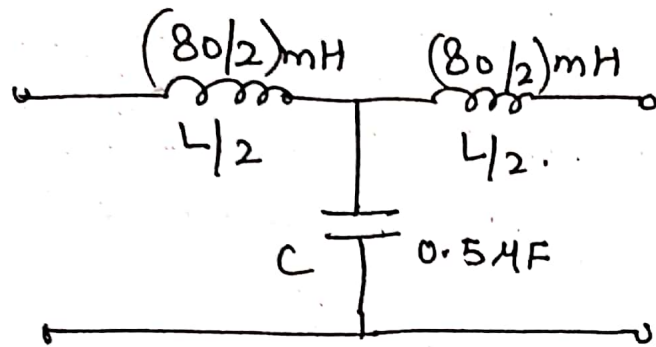Que-9 → Determine the nominal characteristic or design impedance and the cut-off frequency for the filters shown in fig below.



(a) Low pass filter.

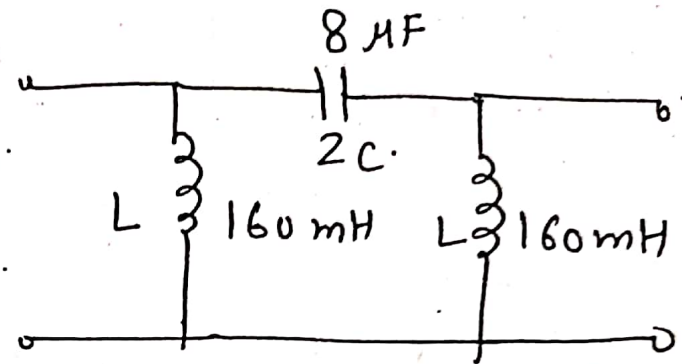

(b) High pass filter.

Que-10 → Design a Constant-K band pass filter with cut-off frequencies of 2 KHz and 5 KHz and nominal characteristic impedance of $R_0 = 600\Omega$.