

Experiment - 6

Aim: Interconnection of two 2-port networks in series-series interconnection and determination of overall z parameter. Also verification of the result.

Apparatus and auxiliaries:


D.C. Power Supply (Variable), Carbon Resistors of 1 k ohm and $Y_{4W} - 6$, Panel Type DC Voltmeter (0-20 V), panel type DC Ammeter (0-25 mA), connecting wires of Patch cords

Theory:

A complicated circuit can be viewed as an interconnection of two or more, similar or dissimilar types of network (called basic building blocks) such that the analysis of an circuit can be easily carried out by expressing the input and output quantities in the form of two simple equations when these simple equations are those pertaining to z parameter, and the currents in each of the building block on input side is same and the current on output side is also same, the interconnection is known as series-series interconnection

Procedure:

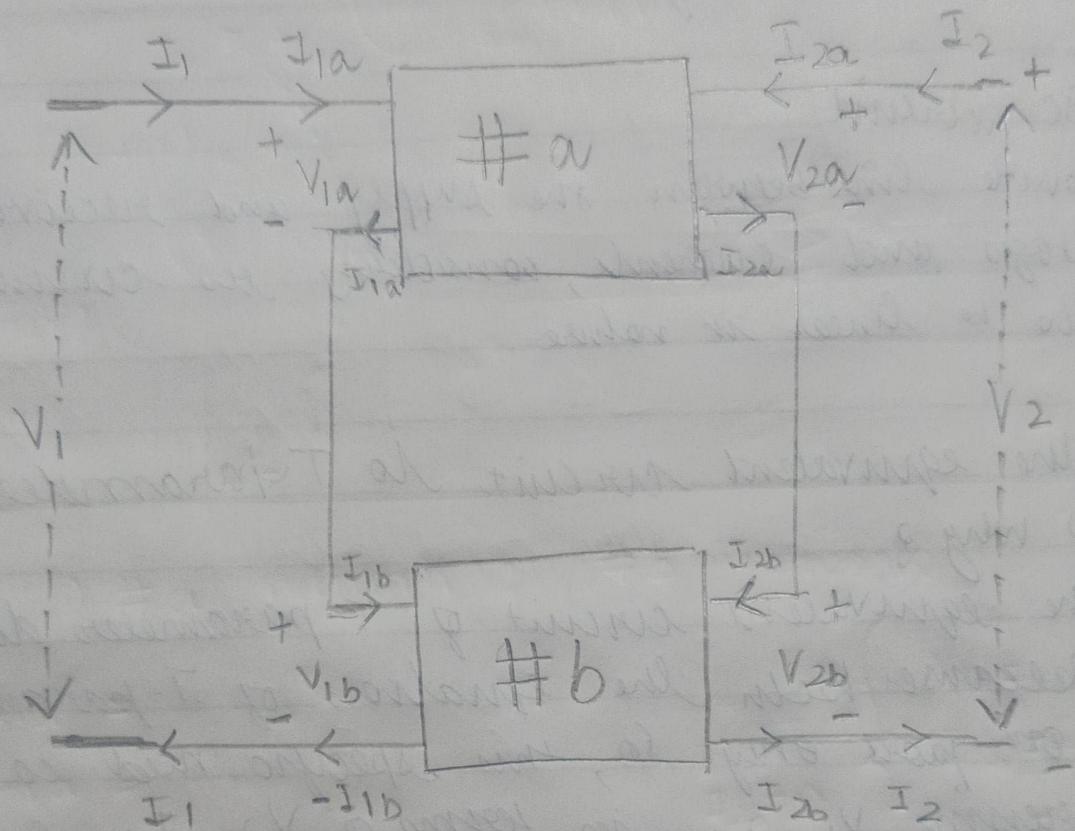Aim: Interconnection of 2 z-parameter network in series
 series interconnection and determination of overall z parameters. Also verification of the result.



SERIES - SERIES INTERCONNECTION

$$\rightarrow V_1 = V_{1a} + V_{1b} \text{ and } \rightarrow V_2 = V_{2a} + V_{2b}$$

$$\rightarrow I_1 = I_{1a} = I_{1b} \rightarrow I_2 = I_{2a} = I_{2b}$$

Connect the circuit as shown in steps 1, 2, 3, 4, 5 and 6.

Result:

By Observation

$$[Z] = \begin{bmatrix} 3.83 & 2.2 \\ 1.67 & 4.8 \end{bmatrix}$$


all in $\text{k}\Omega$

By Calculation

$$[Z] = \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$$

Theoretical Verification:

Applying
KVL in 2 loops

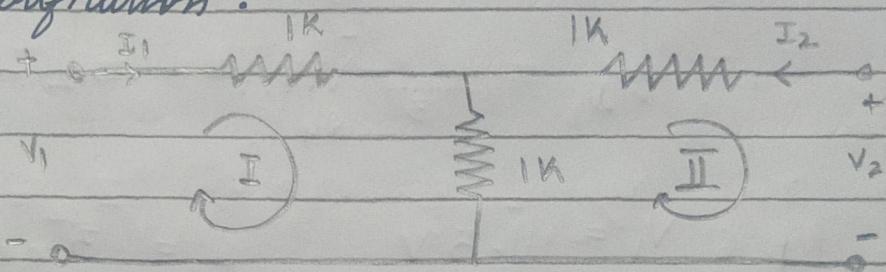

Applying KVL in loop I

$$V_1 - I_1 \times 1 - 1 \times (I_1 \times I_2) = 0$$

where I_1 and I_2 are in mA

$$\Rightarrow V_1 = dI_1 + I_2 - \textcircled{1}$$

Applying KVL in loop II

$$V_2 - I_2 \times 1 - 1 (I_1 + I_2) = 0$$

$$\Rightarrow V_2 = I_1 + dI_2 - \textcircled{2}$$

Z parameter equations $\Rightarrow V_1 = Z_{11}I_1 + Z_{12}I_2 - \textcircled{3}$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 - \textcircled{4}$$


Comparing $\textcircled{1}$ and $\textcircled{3}$

$$Z_{11} = d\text{k}\Omega$$

$$Z_{12} = 1\text{k}\Omega$$

Procedure :

Step 1 and 2 : - trimmable

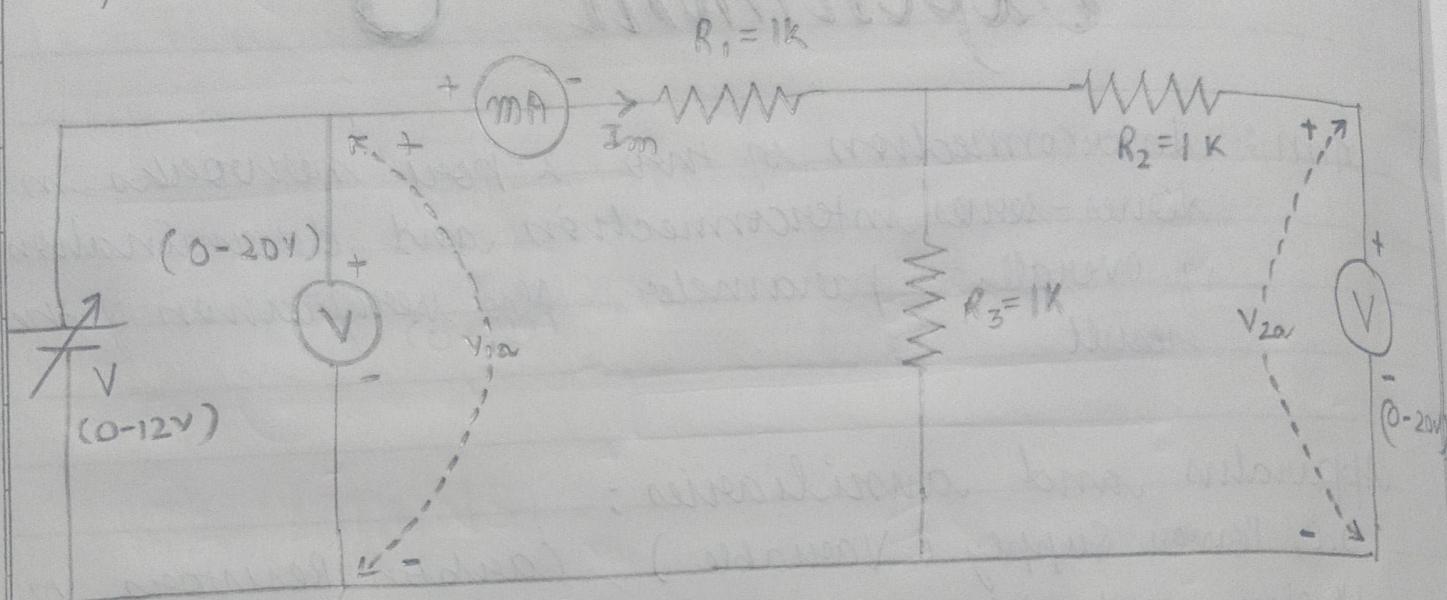


1) #a network ; #b network

$$\left\{ \begin{array}{l} V_{1a} = 11.5V \\ I_{1a} = 5mA \\ I_{2a} = 0 \end{array} \right.$$

$$V_{2a} = 15V$$

$$\text{with } I_{2b}=0 \quad \left\{ \begin{array}{l} V_{1b} = 11.5V \\ I_{1b} = 5mA \\ V_{2b} = 5V \end{array} \right.$$

Step 3 and 4 :

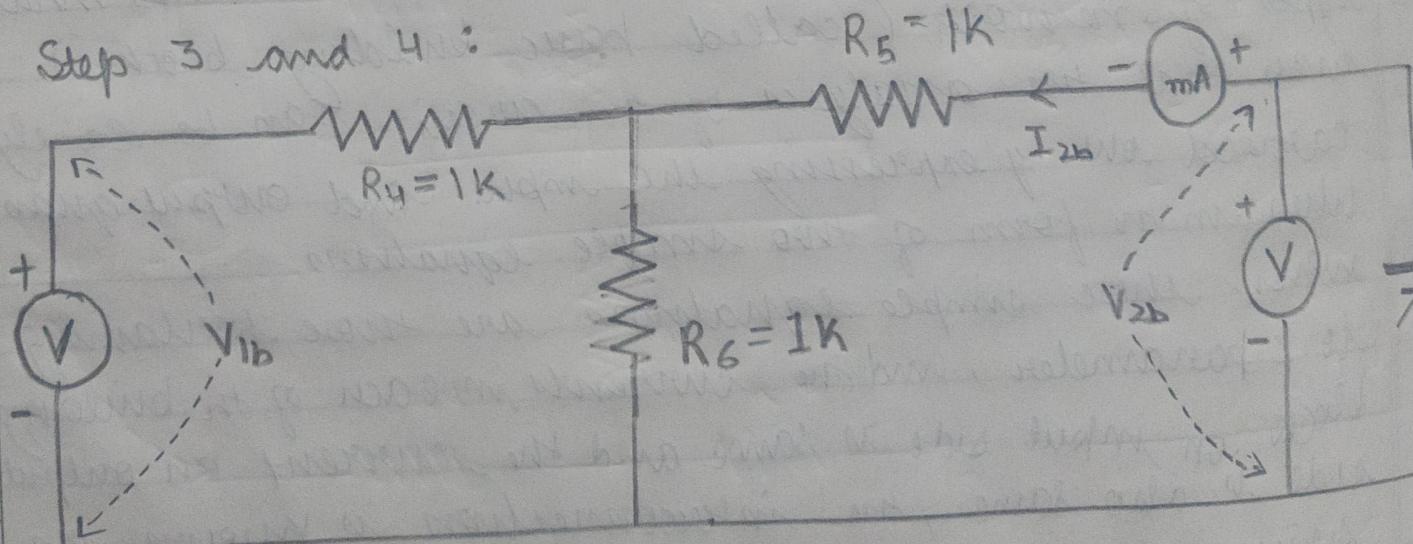

2) #a network ; #b network

Comparing ⑩ and ⑪

$$Z_{11} = 1K$$

$$Z_{22} = 2K$$

Precautions :


- 1) Never connect ammeter directly across the supply.
- 2) Keep the pot of the power supply at zero position initially and gradually increase the voltage.
- 3) Connecting wires must be properly connected.
- 4) Don't pull the connecting cords as it would get damaged.

Sources of Error :

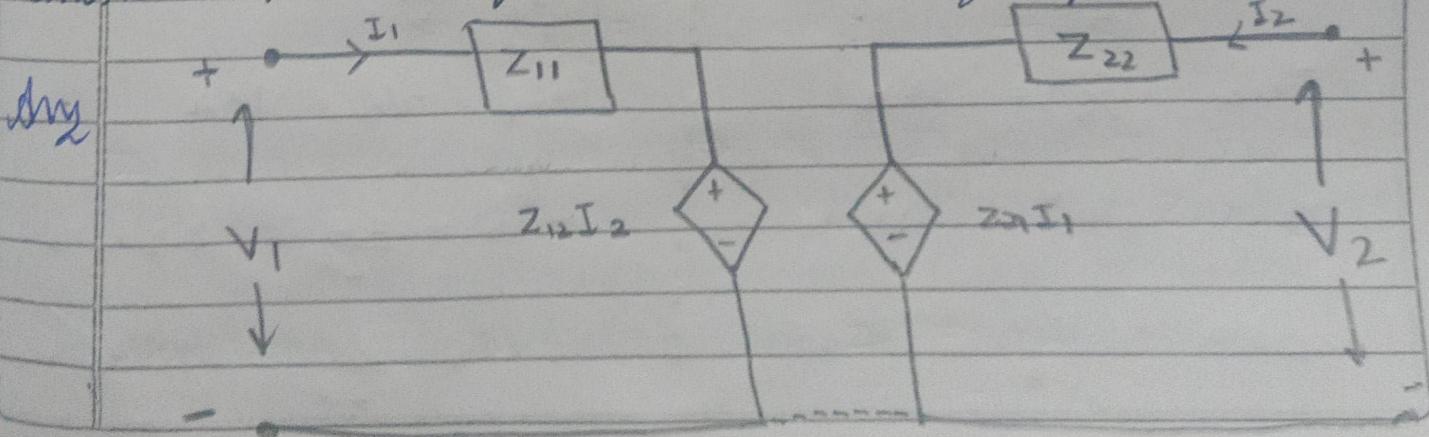- 1) Parallax error in taking readings.
- 2) zero error of instruments
- 3) The resistance of connecting wires.
- 4) The internal resistance of the supply.
- 5) High I.C. of the instruments

VIVA - VOCE

Ans. Draw the equivalent circuit of Z-parameter.




with $I_{1a} = 0$

$$\left\{ \begin{array}{l} V_{2a} = 11.5V \\ I_{2a} = 5mA \\ V_{1a} = 5.5V \end{array} \right.$$

with $I_{1b} = 0$


$$\left\{ \begin{array}{l} V_{2b} = 11.5V \\ I_{2b} = 5mA \\ V_{1b} = 5.5V \end{array} \right.$$

Step 5

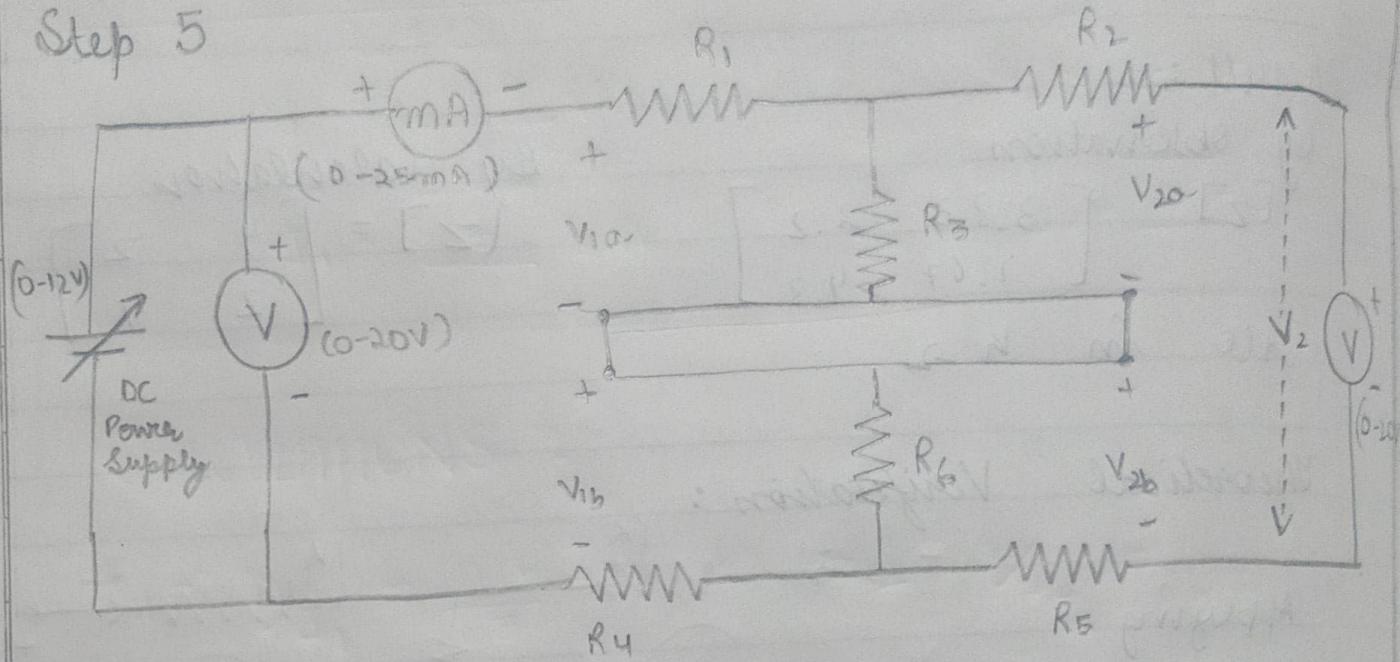

$$V_1 = 11.5V \quad I_1 = 3mA \quad V_2 = 5V$$

Step 6

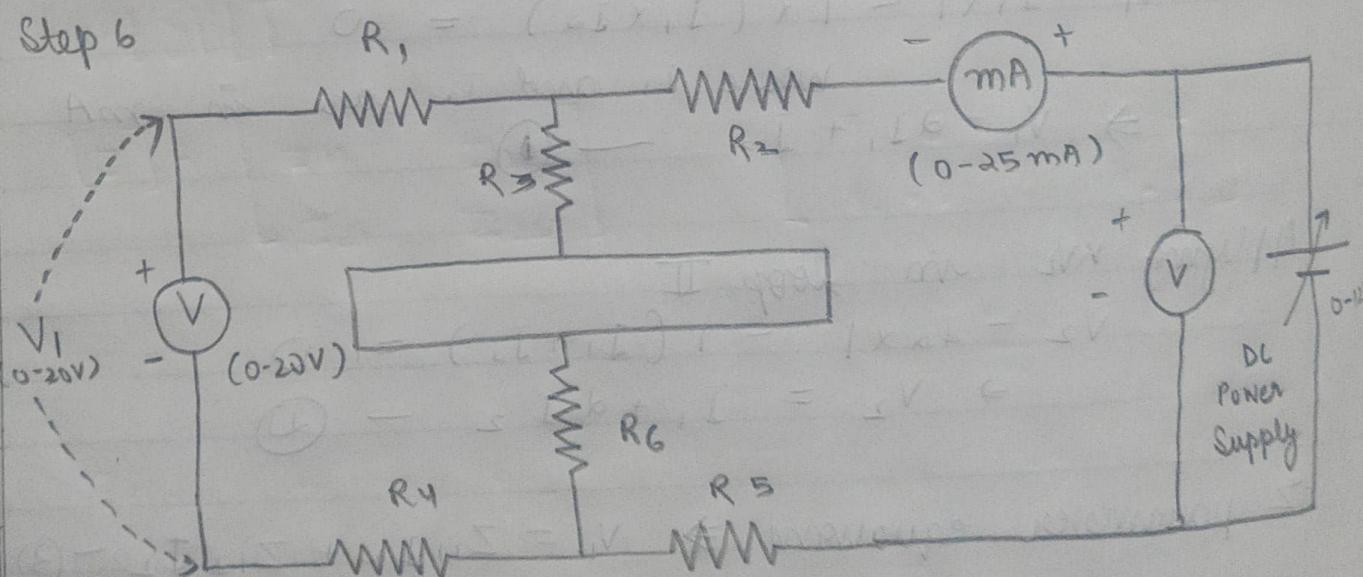

$$I_2 = 2.5mA \quad V_2 = 12V \quad V_1 = 5.5V$$

Ques 2. Why is it necessary to connect common terminals together in series interconnection?

Ans It is necessary because this has an effect of increasing overall voltage and capacity remains the same

Ques 3. What would happen if series-series interconnection is carried out without taking laterally inverted network of second network?

Ans By lateral inversion of second network, the output voltage increases but without it, the overall voltage can't be increased

Ques 4. Show that in the series-series interconnection the Z-parameter matrices get added up.

Ans The Z parameter of the series connected combined network can be written as

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

where,

$$Z_{11} = Z_{11a} + Z_{11b} \quad Z_{21} = Z_{21a} + Z_{21b}$$

$$Z_{12} = Z_{12a} + Z_{12b} \quad Z_{22} = Z_{22a} + Z_{22b}$$

or in matrix form

$$[Z] = [za] + [zb]$$

Ques 5. Give some examples where two or more networks are connected in series-series pattern.

Observation Table :

When output port is open	When input port is open
$I_2 = 0$	$I_1 = 0$
$V_1 = \frac{11.5}{3} V$	$V_2 = \frac{12}{2.5} V$
$V_2 = \frac{5}{3} V$	$V_1 = \frac{5.5}{2.5} V$
$I_1 = 3 \text{ mA}$	$I_2 = 2.5 \text{ mA}$

CALCULATIONS :

$$Z_{11} = \frac{V_1}{I_1} = \frac{11.5}{3} = 3.83 \text{ k}\Omega \quad | \quad Z_{12} = \frac{V_1}{I_2} = \frac{5.5}{2.5} = 2.2 \text{ k}\Omega$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{5}{3} = 1.67 \text{ k}\Omega \quad | \quad Z_{22} = \frac{V_2}{I_2} = \frac{12}{2.5} = 4.8 \text{ k}\Omega$$

RESULT :

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 3.83 & 2.2 \\ 1.67 & 4.8 \end{bmatrix} \text{ All in k}\Omega$$

$$Z_{11a} = \frac{11.5}{5} = 2.3 \text{ k}\Omega$$

$$Z_{11b} = \frac{11.5}{5} = 2.3 \text{ k}\Omega$$

$$Z_{21a} = \frac{5}{5} = 1 \text{ k}\Omega$$

$$Z_{21b} = \frac{5}{5} = 1 \text{ k}\Omega$$

$$Z_{12a} = \frac{5.5}{5} = 1.1 \text{ k}\Omega$$

$$Z_{12b} = \frac{5.5}{2.5} = 2.2 \text{ k}\Omega$$

$$Z_{22a} = \frac{11.5}{5} = 2.3 \text{ k}\Omega$$

$$Z_{22b} = \frac{12}{2.5} = 4.8 \text{ k}\Omega$$

Ques 5. It is used in cascade connections, electronic circuits, communication systems, electrical power system, etc.

Ans 6. With the help of interconnection of two or more networks, show that series-series interconnection is best suited where Z -parameters play an important role.

Why As from the circuit we can see that

$$[Z] = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix}$$

Hence, the Z -parameter play an important role for series-series interconnection, they are the sum of Z -parameters of the individual networks in series.

Ques 7. How will you connect two lattice networks in series-series fashion, assuming that you have an AC source.

A₇ Applying an AC to series-series interconnection will result in same connection but the values will be changed.

By Observation

$$[Z] = \begin{bmatrix} 3.83 & 2.2 \\ 1.69 & 4.8 \end{bmatrix}$$


All in $\times 5\Omega$

Actual values for lower section

By Calculations

$$[Z] = \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$$

All in $\times 5\Omega$

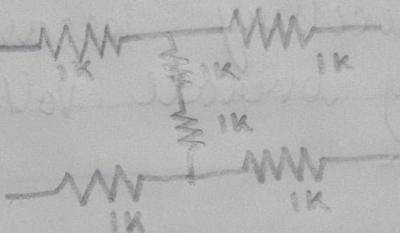

Hence verified.

Equivalent circuit is in terms of Σ and Δ .
In below the equivalent circuit of Σ and Δ is shown.

$$+ b u\Sigma + d u\Sigma = 1V$$

$$\text{Left } [Z] = [\Sigma]$$