

# Experiment - 7

**AIM:** Interconnection of 2 two port network in parallel-parallel interconnections and determination of overall Y-parameter.

**Apparatus required :**

D.C. power supply (variable), carbon resistors of  $1K\Omega$  and  $Y_{4W} - 6$ , Panel type DC voltmeter (0-20V), panel type DC Ammeter (0-25mA), connecting wires and patch cords.

**Theory :**

In a parallel-parallel interconnection both input and output ports are connected in parallel.

The overall Y-parameter matrix for parallel connected two-port network is simply the sum of Y-parameters matrices of each individual two port networks connected in parallel.

$$[Y] = [Y_a] + [Y_b]$$

The figure shows two two-port networks Na and Nb. The resultant of two admittance connection is  $Y_1 + Y_2$ . So, in parallel connection the parameters are Y-parameter.


$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} \quad \text{for network Na}$$

by from Nb

assuming  $V_1 = V_{1a} = V_{1b}$ ;  $V_2 = V_{2a} = V_{2b}$

$$[Y] = [Y_a] + [Y_b]$$

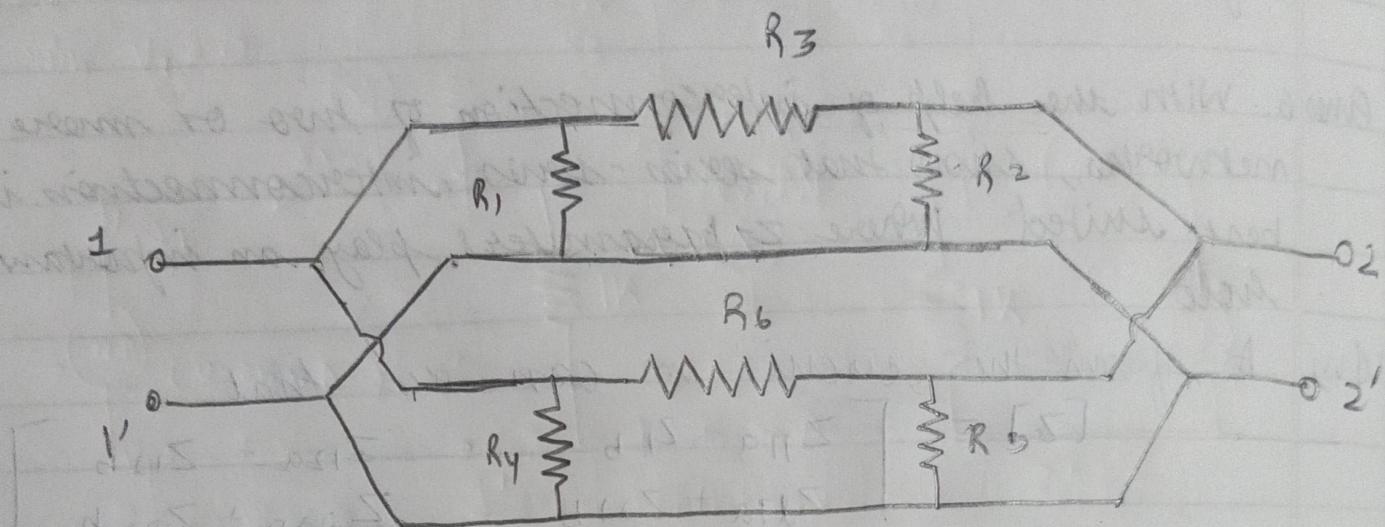
Aim: Interconnection of 2 two-port networks  
in parallel parallel interconnection and  
determination of overall  $y$  parameter



### Parallel-Parallel Interconnection

### # DETERMINATION OF SHORT CIRCUIT ADMITTANCE PARAMETER

with  $V_2 = 0$

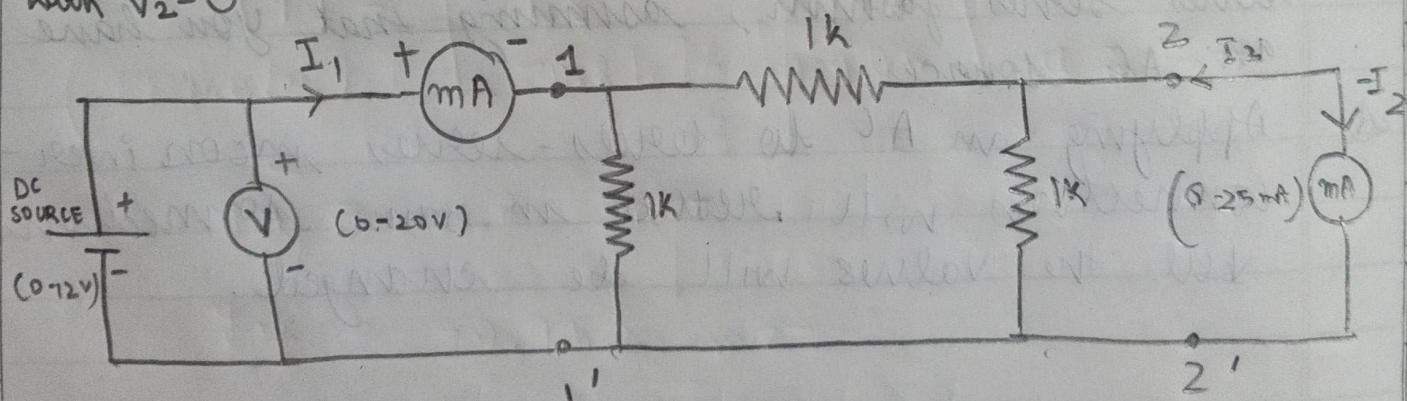

$$V_1 = 7.5 \text{ V}$$

$$I_1 = 13.5 \text{ mA}$$

$$-I_2 = 6 \text{ mA}$$

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned}$$

**Precautions :**

- 1) Never connect ammeter directly across the supply.
- 2) Keep the pot of the power supply at zero position initially and gradually increase its voltage.
- 3) Connecting wires must be properly connected.
- 4) Don't pull the connecting wires hard as it would get damaged.

**Sources of Error :**

- 1) Parallax error in taking readings.
- 2) Zero error of instruments.
- 3) The resistance of connecting wires.
- 4) The internal resistance of the supply.
- 5) High Least Count of the instruments.

**Result :**

By observation,

$$[Y] = \begin{bmatrix} 3.6 & -1.904 \\ -1.6 & 3.810 \end{bmatrix} \quad (\text{mV})$$

By Calculation,

$$[Y] = \begin{bmatrix} 3.7 & -1.72 \\ -1.8 & 3.63 \end{bmatrix} \quad (\text{mV})$$

e), error in each case

$$Y_{11} = 2.78\%$$

$$Y_{12} = 9.67\%$$

$$Y_{21} = 12.5\%$$


$$Y_{22} = 4.72\%$$

$$\text{Error} = \underline{1.85\%}$$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \left( \frac{13.5}{7.5} \right) = 1.8 \text{ mV}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \left( \frac{-6}{7.5} \right) = -0.8 \text{ mV}$$

With  $V_1 = 0$

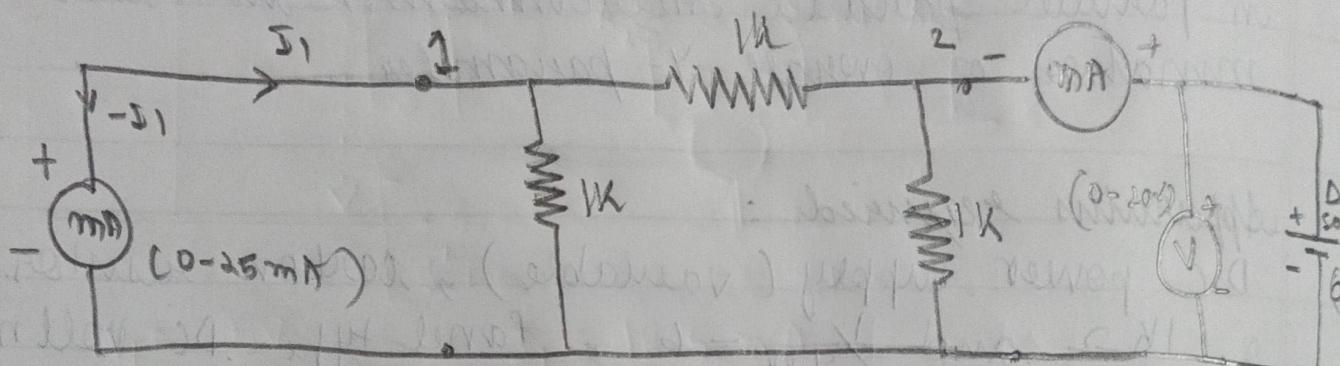

$$V_2 = 10.5 \text{ V}$$

$$I_2 = 20 \text{ mA}$$

$$-I_1 = 10 \text{ mA}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{10}{10.5} = 0.952 \text{ mV}$$

$$[Y] = \begin{bmatrix} 1.8 & -0.952 \\ -0.8 & 1.905 \end{bmatrix} \text{ all in mV}$$


$$Y_{11} = 1.8 \text{ mV} = [1]$$

$$Y_{12} = -0.952 \text{ mV}$$

$$Y_{21} = -0.8 \text{ mV}$$

$$Y_{22} = 1.905 \text{ mV}$$

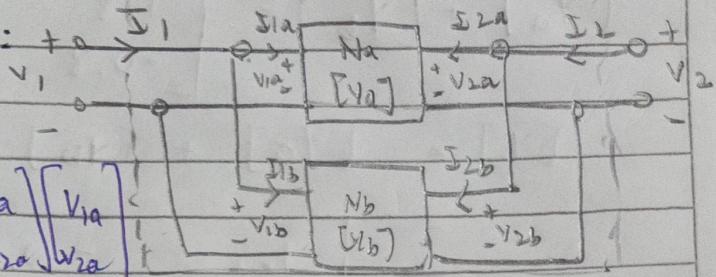Theoretical verification : +  $\xrightarrow{I_1}$



for Network Na,

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

likewise for network Nb,

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

$$V_1 = V_{1a} = V_{1b}, \quad V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b}, \quad I_2 = I_{2a} + I_{2b}$$

$$\text{Now, } I_1 = I_{1a} + I_{1b} = (Y_{11a} V_{1a} + Y_{12a} V_{2a}) + (Y_{11b} V_{1b} + Y_{12b} V_{2b}) \\ = (Y_{11a} + Y_{11b}) V_1 + (Y_{12a} + Y_{12b}) V_2$$

(since  $V_1 = V_{1a} = V_{1b}$  and  $V_2 = V_{2a} = V_{2b}$ )

$$\text{likewise, } I_2 = I_{2a} + I_{2b} = (Y_{21a} + Y_{21b}) V_1 + (Y_{22a} + Y_{22b}) V_2$$

$\Rightarrow$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where

$$Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$


$$Y_{22} = Y_{22a} + Y_{22b}$$

Hence,

$$[Y] = [Y_a] + [Y_b]$$

VIVA VOCE

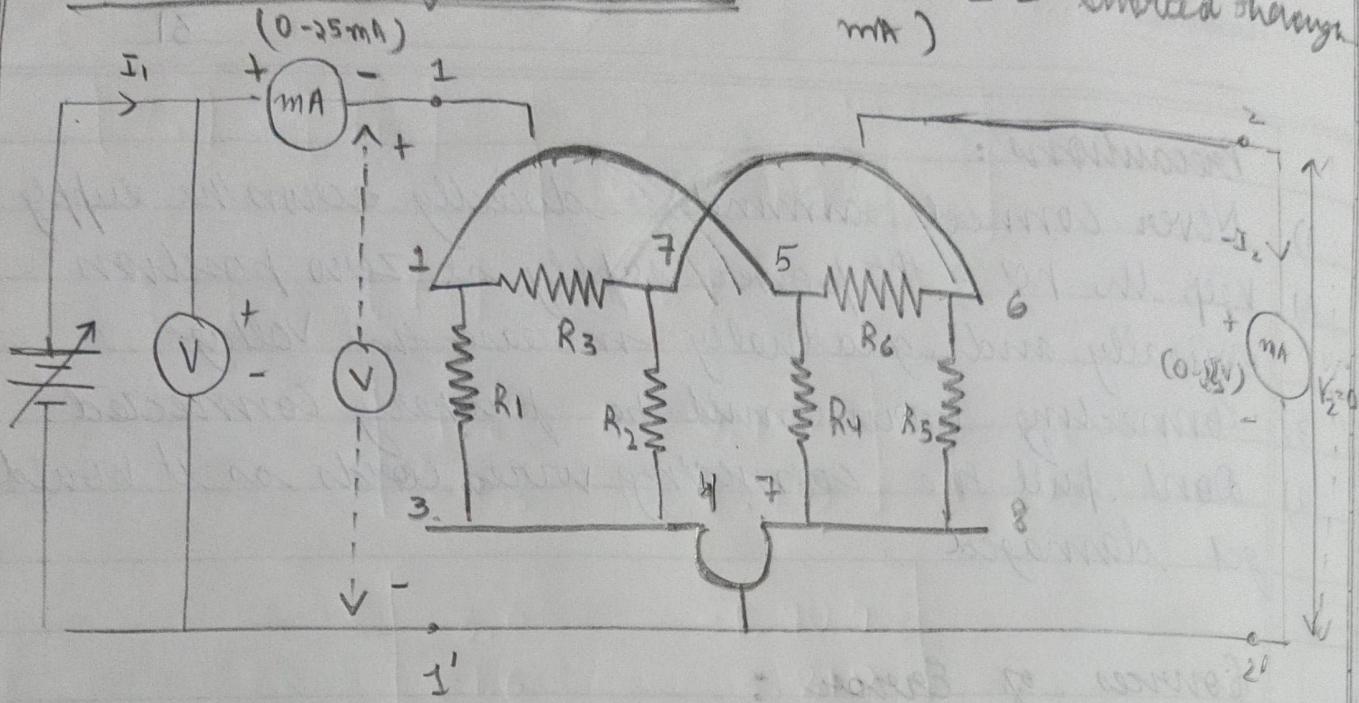Connection diagram on kit (with 2-2' shorted through mA)



$$V_1 = 5V$$

$$I_1 = 18.5 \text{ mA}$$

$$-I_2 = 9 \text{ mA}$$

### OBSERVATION FOR DIRECT CALCULATION

$$\text{For } V_1 = 0 \quad V_2 = 5.5 \text{ V}$$

$$I_2 = 20 \text{ mA}$$

$$-I_1 = 9.5 \text{ mA}$$

$$\text{For } V_2 = 0 \quad V_1 = 5V$$


$$I_1 = 18.5 \text{ mA}$$

$$-I_2 = 9 \text{ mA}$$

$$[8][Y] = \begin{bmatrix} 3.7 & -1.72 \\ -1.8 & 3.63 \end{bmatrix} \quad \text{all in } (\text{m}^{\frac{1}{2}})$$

observed

$$\begin{bmatrix} 4 & -2 \\ -2 & 4 \end{bmatrix}$$

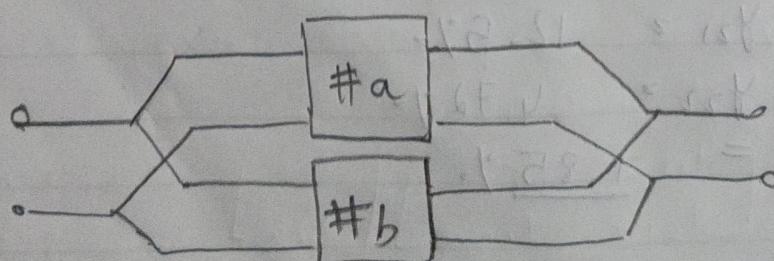

Ans 1. Is it preferable to connect bulbs in series?

Ans No, its preferred to connect them in parallel so that if one bulb blow out others continue to get a current supply.

Ans 2. What is the short circuit admittance of composite network and how is it evaluated?

Ans Short circuit admittance of a composite network is sum of short circuit admittance of each individual networks

$$[Y_{total}] = [Y_1] + [Y_2] + [Y_3] + \dots + [Y_n]$$

Ans 3. What are the applications of parallel network?

Ans They are used in dc supply from automobile industry, computer hardware etc.

Ans 4. Why study of 2-port network is important?

Ans Two port network model is used in circuit analysis techniques to isolate portions from a larger circuit. This allows response of network to signal applied to ports to be calculated easily without solving for all internal voltages and currents in the network.

## Result Obtained Using Property of Interconnection

$$[Y_a] = [Y_b] = \begin{bmatrix} 1.8 & -0.952 \\ -0.8 & 1.905 \end{bmatrix}$$

$$[Y] = [Y_a] + [Y_b]$$

$$= \begin{bmatrix} 1.8 & -0.952 \\ -0.8 & 1.905 \end{bmatrix} + \begin{bmatrix} 1.8 & -0.952 \\ -0.8 & 1.905 \end{bmatrix}$$

$$= \begin{bmatrix} 3.6 & -1.904 \\ -1.6 & 3.810 \end{bmatrix}$$

## COMPARISON OF EXPERIMENTAL RESULTS :

Direct calculation  $[Y] = \begin{bmatrix} 3.7 & -1.72 \\ 1.88 & 3.263 \end{bmatrix}$  (mV)

Using property  $[Y] = \begin{bmatrix} 3.6 & -1.904 \\ -1.6 & 3.810 \end{bmatrix}$  (mV)

∴ error in each case

$$Y_{11} = 1\% \quad 2.78\%$$

$$Y_{12} = 9.67\%$$

$$Y_{21} = 12.5\%$$

$$Y_{22} = 4.72\%$$

avg error =  $\frac{1.85\%}{[Y] + 6P}$

300V / 400V