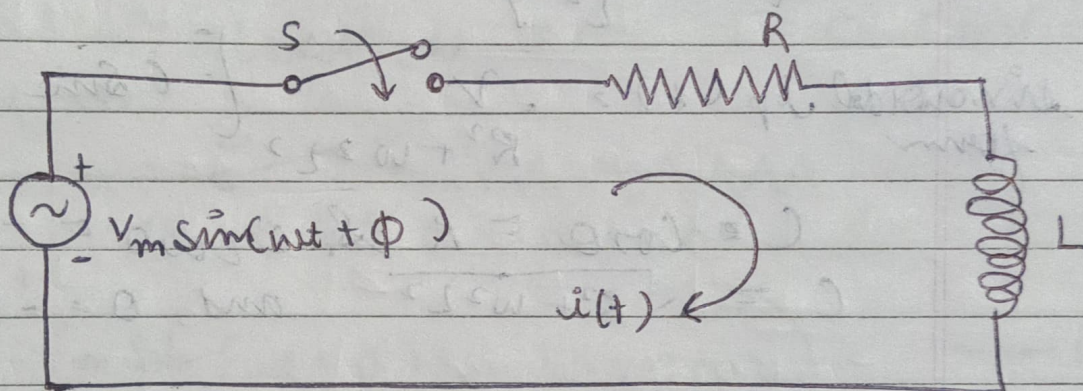


CIRCUIT SYSTEM

→ Transient Response of R-L circuit having sinusoidal

Q Consider a series R-L circuit excited by a sinusoidal voltage source as shown in fig. below. The switch 'S' is closed at time $t = 0$. Find the response (current $i(t)$)



Ans Applying KVL,

$$L \frac{di(t)}{dt} + R i(t) = v_m \sin(\omega t + \phi) \quad \text{--- (1)}$$

The complementary funcⁿ of eqⁿ (1) is

$$i_c(t) = x e^{R/L t}$$

finding integral of eqⁿ (1)

$$i_p(t) = e^{R/L t} \int \frac{v_m}{L} \sin(\omega t + \phi) \cdot e^{-R/L t} dt$$

$$= \frac{v_m}{2jL} e^{-R/L t} \int \{ e^{j(\omega t + \phi)} - e^{-j(\omega t + \phi)} \} e^{R/L t} dt$$

$$= \frac{v_m}{2jL} e^{R/L t} \left[\frac{e^{j(\omega t + \phi) + R/L t}}{j\omega + R/L} - \frac{e^{-j(\omega t + \phi) + R/L t}}{-j\omega + R/L} \right]$$

$$\frac{V_m \sin \phi}{R} = k + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin(\phi + \tan^{-1} \frac{1}{\omega CR})$$


$$i(t) = \left[\frac{V_m \sin \phi}{R} - \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin(\phi + \tan^{-1} \frac{1}{\omega CR}) \right] e^{-\frac{t}{RC}} + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin(\omega t + \phi + \tan^{-1} \frac{1}{\omega CR})$$

$$i(t) = \left[\frac{V_m \sin \phi}{R} - \frac{V_m \sin(\phi + \theta)}{Z} \right] e^{-\frac{t}{RC}} + \frac{V_m \sin(\omega t + \phi + \theta)}{Z}$$

where $\theta = \tan^{-1} \frac{1}{\omega CR}$

$$Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \text{ : impedance}$$

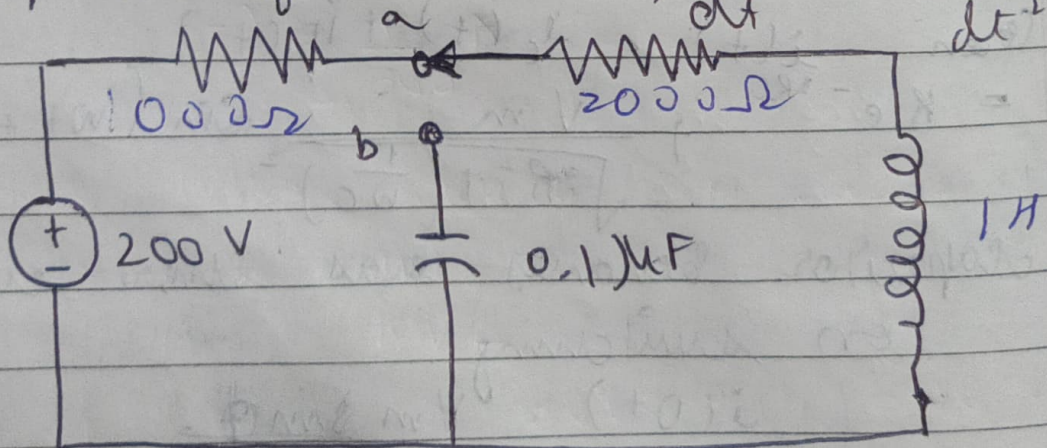Ques 3. In the given circuit shown the switch S is changed from position a to b at time $t = 0$. Find out an expression for current $i(t)$, $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t = 0^+$



100

At position a :

Steady state value of current $i(0^-)$:-

$$i(0^-) = \frac{200}{1000 + 2000} = \frac{2}{30} = \frac{1}{15} \text{ A}$$

At position b :

$$i(0^+) = i(0^-) = 0.0666 \text{ A or } \frac{1}{15} \text{ A}$$

Applying KVL :
$$2000 i(t) + 1 \cdot \frac{di(t)}{dt} = 1 \quad \int_0^t di(t) dt = 0$$

$$\Rightarrow \frac{di(t)}{dt} + 2000 i(t) = 0 \quad (\because \text{capacitor initially is uncharged ; At } t=0^+ \text{ capacitor s.c.})$$

$$\Rightarrow \frac{di(0^+)}{dt} = -2000 i(0^+) = \frac{-2000}{15} \text{ A/sec}$$

$$\frac{di(0^+)}{dt} = -133.33 \text{ A/sec}$$

diff wrt : t

$$\frac{d^2 i(t)}{dt^2} + 2000 \frac{di(t)}{dt} + 10^7 i(t) = 0$$

$$\Rightarrow \frac{d^2 i(0^+)}{dt^2} = -2000 (-133.33) - 10^7 (0.0666)$$


$$\frac{d^2 i(0^+)}{dt^2} = - \left\{ 2000 \left(\frac{-2000}{15} \right) + \frac{10^7}{15} \right\}$$

$$= - \frac{10^6}{15} \{ -4 + 10 \} = - \frac{10^6}{15} \{ -4 + 10 \}$$

$$= -\frac{6}{15} \text{ sec}$$

$$\Rightarrow \frac{d^2 i(t)}{dt^2} = -4 \times 10^5 \text{ A/sec}^2$$

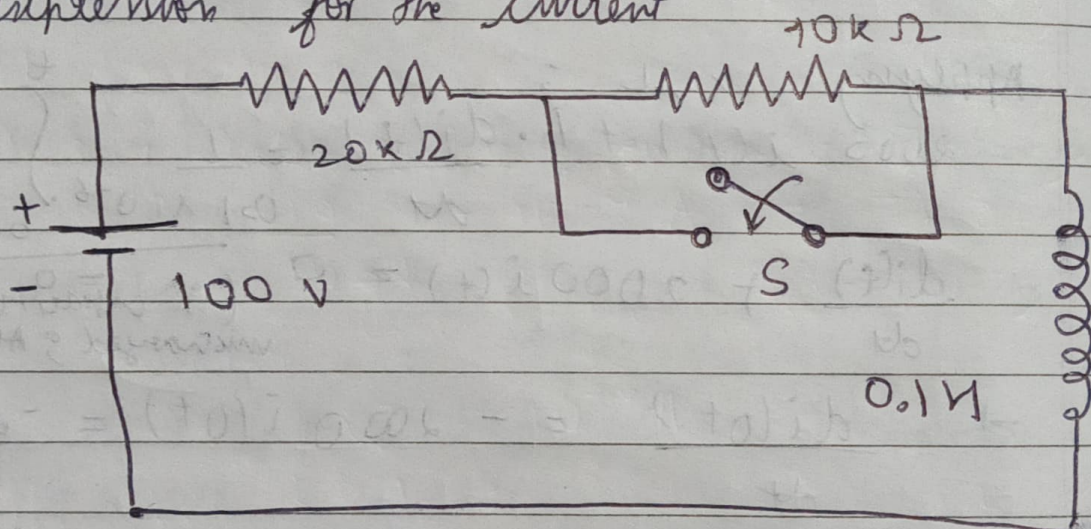Ques 4. A dc voltage of 100V is applied in the adjoining circuit and the switch S is open. The switch S is closed at $t = 0$. Find the complete expression for the current.



Ans

When Switch S was open:

$$\text{Steady state current } i(0^-) = \frac{100}{20000 + 10000} \text{ A}$$

(\because Inductor \rightarrow S.C at $t = \infty$)

$$i(0^-) = \frac{1}{300} \text{ A}$$

Now, when switch S is closed at $t = 0$

10Ω Resistance \rightarrow short circuited

Applying

KVL:

$$0.1 \frac{di(t)}{dt} + 20000 i(t) = 100$$

$$\frac{di(t)}{dt} + (2 \times 10^5) i(t) = 10^3$$

Type II
(1st order non homogeneous)
D.E.

⇒ General solution - ①

$$i(t) = \frac{10^3}{2 \times 10^5} + K e^{-(2 \times 10^5)t}$$

Initially conditions $\Rightarrow i(0^+) = i(0^-) = \frac{1}{300} \text{ A}$

$$\frac{1}{300} = \frac{1}{200} + K e^{-(2 \times 10^5)(0)}$$

$$\Rightarrow K = \frac{1}{300} - \frac{1}{200} \Rightarrow K = \frac{-1}{600}$$

$$\therefore \textcircled{1} i(t) = \frac{1}{200} - \frac{1}{600} e^{-(2 \times 10^5)t}$$

$$A \Rightarrow i(t) = \frac{10}{2} \left(1 - \frac{1}{3} e^{-200t} \right) \text{ mA}$$

msec

$$i(t) = 5 \left(1 - \frac{1}{3} e^{-200t} \right)$$


$i(t) \rightarrow \text{mA}$
 $t \rightarrow \text{msec}$

$$i(0) = 66.6 \text{ mA} - 133.2 \text{ A/sec}$$

$$\frac{d^2 i(t)}{dt^2} = -400 \times 10^3 \text{ A/sec}^2$$

Ques 3. In the circuit, the switch is moved from position 1 to 2 at $t = 0$. Determine i , $\frac{di}{dt}$ and $\frac{d^2 i}{dt^2}$ at $t = 0^+$.

Ans

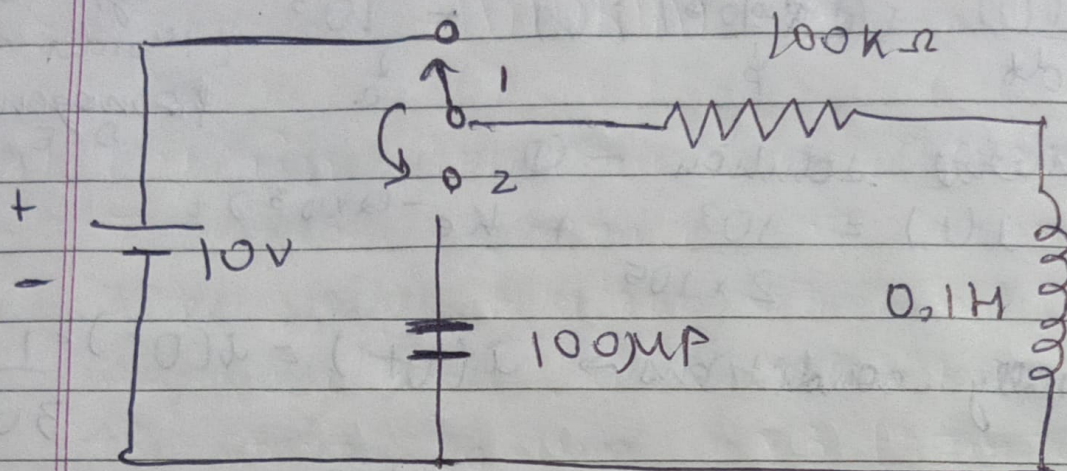

At position 1 :

steady state value of current $i(0^-)$ \therefore
 $i(0^-) = \frac{10}{100k} = 10^{-4} \text{ A} \Rightarrow i(0^-) = 0.1 \text{ mA}$

At position 2 :

$$i(0^+) = i(0^-) = 10^{-4} \text{ A}$$

Applying KVL :

$$(100 \times 10^3) i(t) + 0.1 \frac{di(t)}{dt} + \int_0^t i(t) dt = 0$$

\nearrow

$$\frac{d(i(t))}{dt} + (10^6) i(t) = 0$$

$$\frac{di(0^+)}{dt} = -10^6 (10^{-4}) = -10^2 \text{ A/sec}$$

$$\frac{d^2 i(t)}{dt^2} + 10^6 \frac{di(t)}{dt} + 10^5 i(t) = 0$$

$$\therefore \frac{d^2 i(0^+)}{dt^2} = -10^6 (10^2) - 10^5 (10^{-4})$$

$$\Rightarrow \frac{d^2 i(0+)}{dt^2} = -(10^8 + 10) \text{ A/sec}^2$$

$$\frac{d^2 i(0+)}{dt^2} \approx -10^8 \text{ A/sec}^2$$