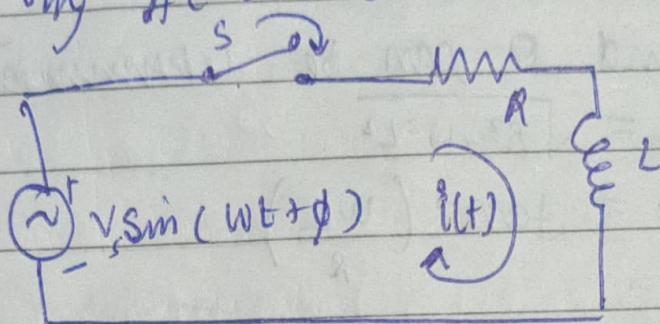


Name - Syeda Reeha Anasar
 Roll no. - 14124802719

Ques. Transient response of series RL circuit having AC excitation



applying KVL,

$$L \frac{di}{dt} + Ri(t) = V_m \sin(\omega t + \phi)$$

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_m}{L} \sin(\omega t + \phi) \quad \text{--- (1)}$$

This is non-homogeneous eqⁿ. The current $i(t)$ consists of sum of complementary function $i_c(t)$ and particular integral $i_p(t)$ i.e.

$$i(t) = i_c(t) + i_p(t)$$

$$i_c(t) = K e^{-R/L t}$$

and particular integral of eqⁿ

$$i_p(t) = e^{-R/L t} \int \frac{V_m \sin(\omega t + \phi)}{L} e^{R/L t} dt$$

$$i_p(t) = \frac{V_m e^{-R/L t}}{2jL} \left[\frac{e^{j(\omega t + \phi) + R/L t}}{j\omega + R/L} - \frac{e^{-j(\omega t + \phi) + R/L t}}{-j\omega + R/L} \right]$$

$$= \frac{V_m}{2jL} \left[\frac{e^{j(\omega t + \phi)}}{j\omega + R/L} - \frac{e^{-j(\omega t + \phi)}}{-j\omega + R/L} \right]$$

$$= \frac{V_m}{2jL} \left[\frac{e^{j(\omega t + \phi)}(-j\omega + R/L) - e^{-j(\omega t + \phi)}(j\omega + R/L)}{(j\omega + R/L)(-j\omega + R/L)} \right]$$

$$= \frac{V_m}{L} \left[\frac{R/L \sin(\omega t + \phi) - \omega \cos(\omega t + \phi)}{\omega^2 + R^2/L^2} \right]$$

$$= \frac{V_m}{R^2 + \omega^2 L^2} (A \sin(\omega t + \phi) - \omega L \cos(\omega t + \phi))$$

~ This can be reduced to single sinusoidal in the form,

$$i_p(t) = \frac{V_m}{R^2 + \omega^2 L^2} \left(C \sin(\omega t + \phi + 0) \right)$$

where C and O can be determined as

$$C = \sqrt{R^2 + W^2 L^2}$$

$$\theta = \tan^{-1} \left(\frac{WL}{R} \right)$$

Sub C and D

$$i_p(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cdot \sin\left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}\right)$$

$$2. \quad i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi + \tan^{-1} \frac{\omega L}{R}) + k e^{-\frac{R}{L}t}$$

Since inductor behaves as an open circuit
At switching.

$$i(0^+) = 0$$

$$0 = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\phi - \tan^{-1} \frac{\omega L}{R} \right) + k$$


$$V_L = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\phi - \tan^{-1} \frac{\omega L}{R} \right)$$

$$i(t) = \frac{V_m}{Z} (\sin(\omega t + \phi + \theta) - \sin(\phi + \theta) e^{-R/L t})$$

$$\theta = -\tan^{-1} \frac{\omega L}{R} \quad Z = \sqrt{R^2 + \omega^2 L^2}$$

TRANSIENT RESPONSE OF SERIES RC CIRCUIT

HAVING SINUSOIDAL EXCITATION :

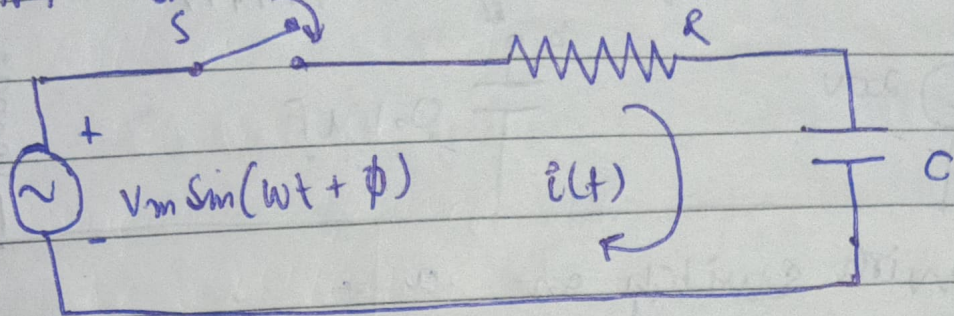

Applying KVL \Rightarrow

$$Ri(t) + \frac{1}{C} \int_0^t i(t) dt + v_c(0^+) = V_m \sin(\omega t + \phi)$$

On differentiating \Rightarrow

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = \frac{V_m \omega \cos(\omega t + \phi)}{R}$$

General solⁿ $i(t) = i_c(t) + i_p(t)$

$$= k e^{-t/RC} + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\omega t + \phi + \tan^{-1} \frac{1}{\omega CR}\right)$$

Since capacitor behaves as short circuit at switching

$$i(0^+) = \frac{V_m \sin \phi}{R}$$


$$\frac{V_m \sin \phi}{R} = k + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left[\phi + \tan^{-1} \frac{1}{\omega CR}\right]$$

$$k = \frac{V_m \sin \phi}{R} - \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\phi + \tan^{-1} \frac{1}{\omega CR}\right)$$

$$i(t) = \left[\frac{V_m \sin \phi}{R} - \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\phi + \tan^{-1} \frac{1}{\omega CR}\right) \right] e^{-t/RC} + \frac{V_m}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin\left(\omega t + \phi + \tan^{-1} \frac{1}{\omega CR}\right)$$

$$i(t) = \left[\frac{V_m \sin \phi}{R} - \frac{V_m \sin(\phi + \theta)}{2} \right] e^{-t/RC} + \frac{V_m \sin(\omega t + \phi + \theta)}{2}$$
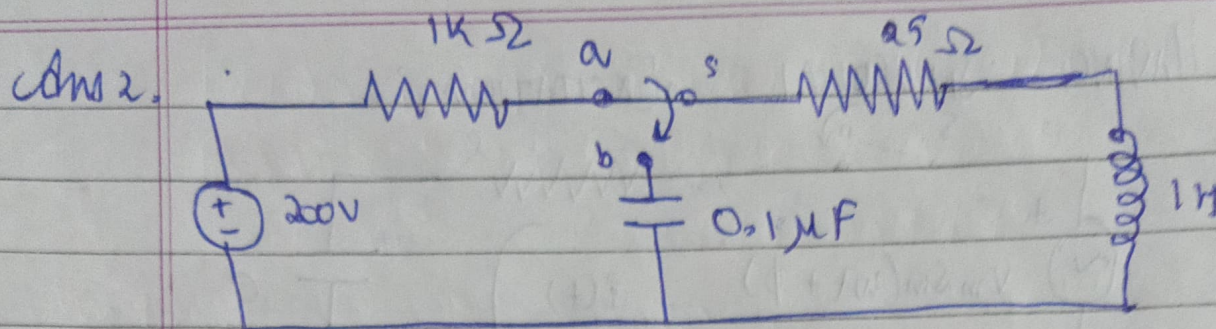
$$\theta = \tan^{-1} \left(\frac{1}{\omega CR} \right) \quad \text{or} \quad Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$



with switch on 'a'.

$$i(0^-) = \frac{200}{3000} = \frac{2}{30} = 0.06 \text{ A}$$

when switch on 'b'

$$i(0^+) = i(0^-) = 0.06 \text{ A}$$

Applying, KVL,

$$\frac{di(t)}{dt} + 2000 i(t) + \frac{1}{0.1 \times 10^{-6}} \int_0^t i(t) dt = 0 \quad \text{--- (1)}$$

Since initial capacitor is uncharged and at switching instant capacitor behaves as short

$$\text{i.e. } \frac{1}{0.1 \times 10^{-6}} \int_0^t i(t) dt = 0$$

then from eqⁿ (1)

$$\frac{di(t)}{dt} + 2000 i(t) = 0$$

$$\frac{di(t)}{dt} = -2000 i(t)$$

$$\frac{di(0^+)}{dt} = -2000 i(0^+) = -2000 \times \frac{0.06}{100} = -120 \text{ A/s}$$


$$\frac{d^2 i(t)}{dt^2} + 2000 \frac{di(t)}{dt} + \frac{1}{0.1 \times 10^{-6}} i(t) = 0$$

$$\frac{d^2 i(0^+)}{dt^2} = -2000 \times (-120) - \frac{1}{0.1 \times 10^{-6}} (-0.06)$$

$$\frac{d^2 i(0^+)}{dt^2} = +240000 - \frac{10^7 \times 6}{100}$$

$$= 240000 - 600000 = 36 \times 10^4 \text{ A/sec}$$

$$= 36 \times 10^4 \text{ A/sec}^2$$

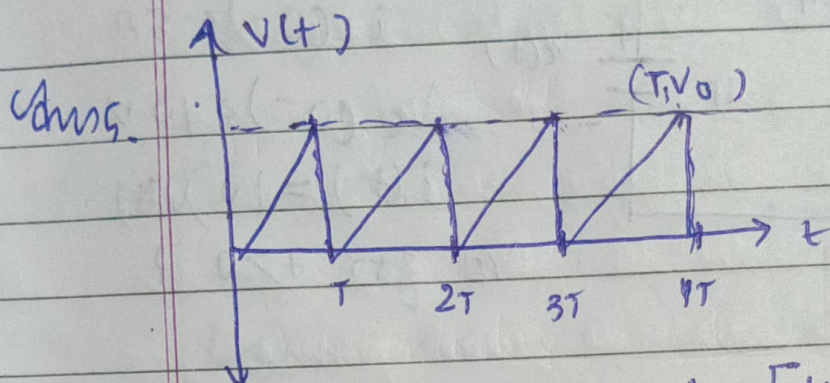

this is a periodic function with period T

Laplace transform first cycle

$$V(t) = 2 \left[\frac{V_0}{T} - t \cdot [u(t) - u(t-T)] \right]$$

$$= \frac{V_0}{T} - \frac{1}{s^2} - 2 \frac{V_0}{T} t u(t-T) = \frac{V_0}{Ts^2} - \frac{V_0}{T} (t-T+T) u(t-T)$$


$$= \frac{V_0}{Ts^2} - \frac{V_0}{T} (t-T) u(t-T) - \frac{V_0}{T} u(t-T)$$

$$= \frac{V_0}{Ts^2} - \frac{V_0}{T} \frac{e^{-Ts}}{s^2} - \frac{V_0}{T} \frac{e^{-Ts}}{s}$$

Laplace transform of periodic function with period T

$$T = \frac{1}{1-e^{-Ts}} = \frac{1}{1-e^{-Ts}} \left(\frac{V_0}{Ts^2} - \frac{V_0}{T} \frac{e^{-Ts}}{s^2} - \frac{V_0}{T} \frac{e^{-Ts}}{s} \right)$$

Ans

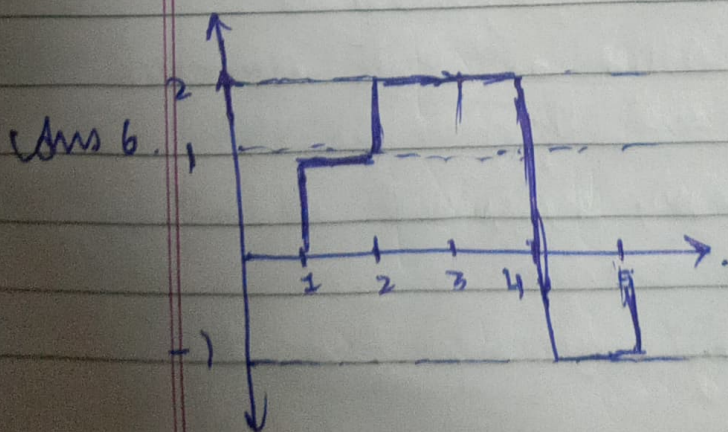


$$F(t) = 1 [u(t-1) - u(t-2)] + 2 [u(t-2) - u(t-4)] - 1 [u(t-4) - u(t-5)]$$

$$F_s(t) = u(t-1) + u(t-2) - 3u(t-4) + u(t-5)$$

$$F(s) = \frac{e^{-s}}{s} + \frac{e^{-2s}}{s} - \frac{3e^{-4s}}{s} + \frac{e^{-5s}}{s}$$

Ans 7.

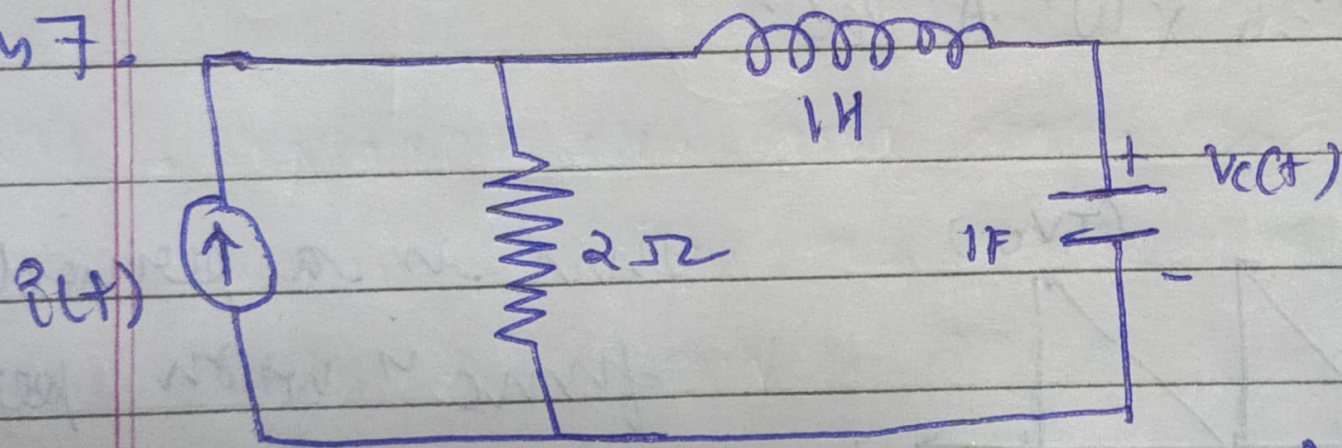

$$i_L(0^-) = 5A$$

$$v_c(0^-) = 10V$$

$$i(t) = 10u(t)$$

v_c for $t > 0$?

$$2(0^+) :$$

KVL,

$$288 V(t) = 24 i_1 + 2 \frac{di_1}{dt} + 80 (i_1 - i_2) \quad \text{--- (1)}$$

$$i_2 = i_1 \cdot \frac{80}{20+80} \quad (\text{By current division rule})$$

$$i_2 = 0.8 i_1$$

$$\begin{aligned} 288 V(t) &= 24 i_1 + 2 \frac{di_1}{dt} + 80 (i_1 - 0.8 i_1) \\ &= 40 i_1 + 2 \frac{di_1}{dt} \end{aligned}$$

inductor
open circuit

$$\frac{di_1}{dt} + 20 i_1 = 144 (V)$$

$$i_1(t) = \frac{144}{20} + k e^{-20t}$$

$t = 0^+$, inductor is open circuit

$$i_1(t) = \frac{144}{20} (1 - e^{-20t}) = 7.2 (1 - e^{-20t})$$

$$i_2(t) = 0.8 i_1(t) = 5.76 (1 - e^{-20t})$$

$$i_1(0^+) = 0$$

$$i_2(0^+) = 0$$

$$V_1(0^+) = 288 V$$


$$i_1(\infty) = 7.2 A$$

$$i_2 = 5.76 A$$


$$V_1(\infty) = 2 \frac{di_1(\infty)}{dt} = 2 \times 0 = 0$$

(steady state)
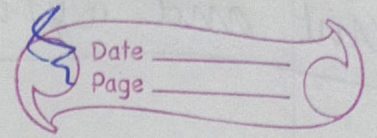
$$V_C = 20 - 10e^{-t} - 5e^{-7t} \text{ V}$$



Ans.

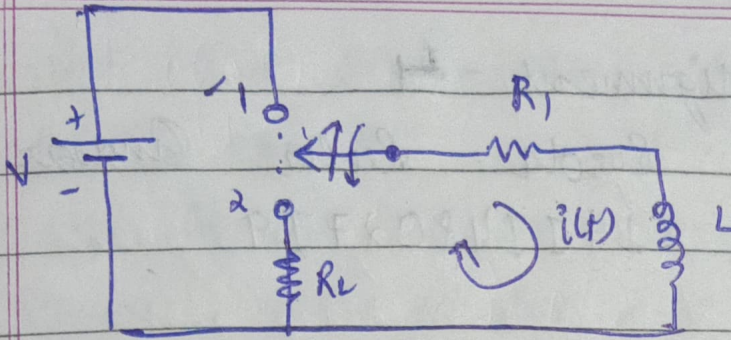

$$i(t) = ?$$

At position ① $i(0^-) = \frac{V}{R_1}$

At position 2, $i(0^+) = i(0^-) = \frac{V}{R_1}$

$$L \frac{di(t)}{dt} + R_1 i(t) + R_2 i(t) = 0$$

$$\frac{di(t)}{dt} + \left(\frac{R_1 + R_2}{L} \right) i(t) = 0 \quad i(t) = R e^{-(R_1 + R_2/L)t}$$

$$i(t) = R e^{-(R_1 + R_2/L)t} \quad i(0^+) = \frac{V}{R_1}$$

$$\frac{V}{R_1} = R$$

$$i(t) = \frac{V}{R_1} e^{-(R_1 + R_2/L)t}$$

Ans