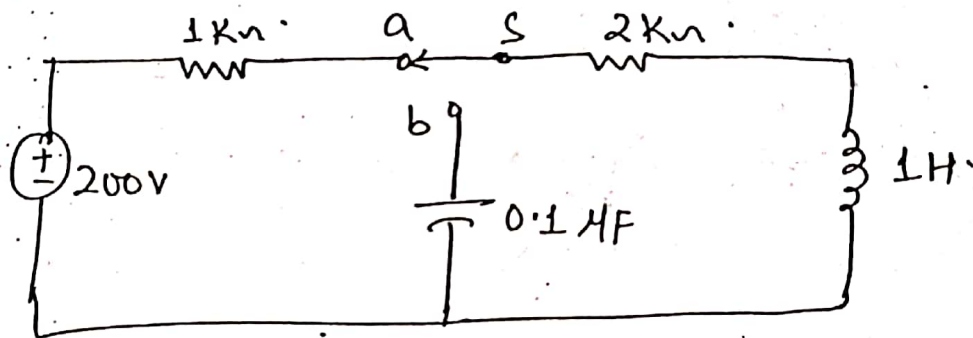


Circuit and Systems


Assignment No. 2

Que-1 Find the transient responses of series R-L and series R-C circuits having sinusoidal excitation.


Que-2 In the given circuit shown in fig. below, the switch S is changed from position 'a' to position 'b' at $t=0$. Find an expression for current $i(t)$, $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t=0^+$



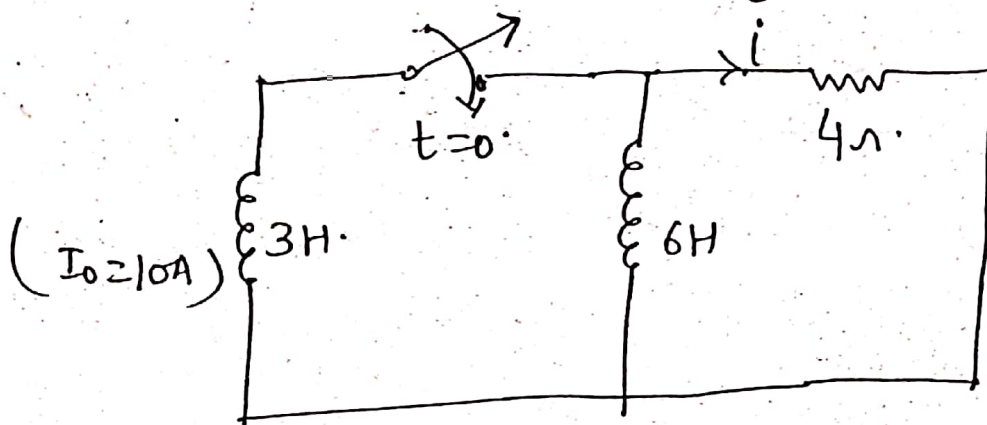
Que-3 A 3-H inductor in the circuit shown in fig. below, carries a 10-A initial current. The switch is closed at $t=0$. Solve for current i .



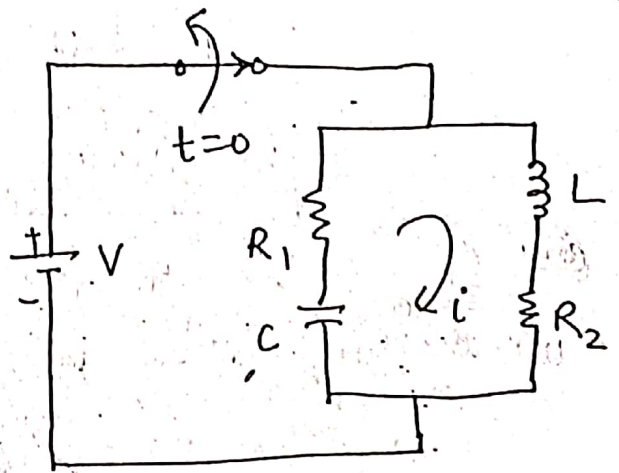
Que-4→ The switch in the circuit shown in fig. is opened at $t=0$. Determine the current ' i ' and its derivative at $t=0^+$



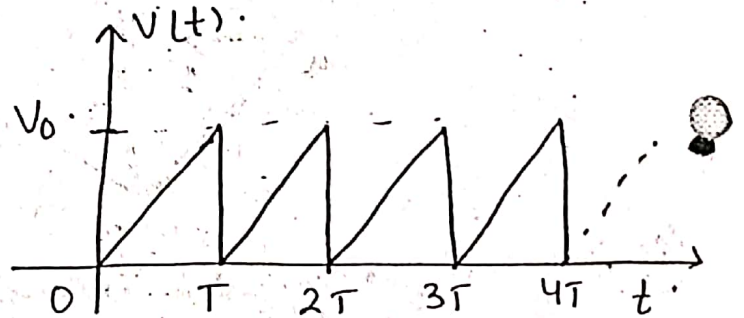
Que-5→ Find the Laplace transform of the waveform shown in figure.



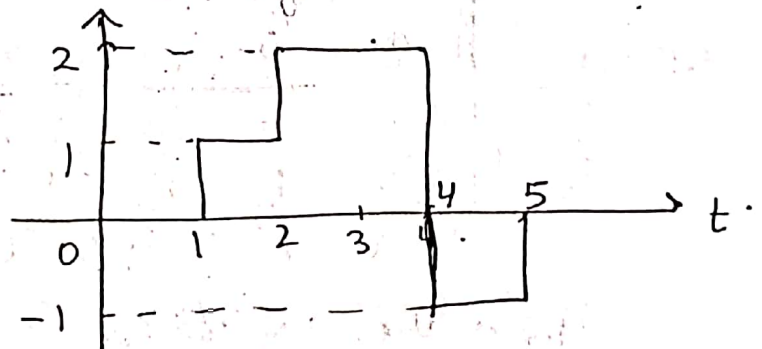Que-6→ Find the Laplace transform of the waveform shown in figure.



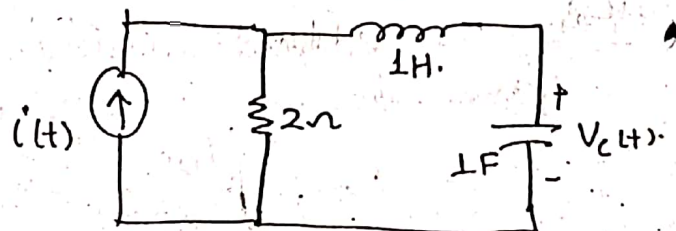Que-7→ In the circuit shown in figure, the initial values are, $i_L(0^-) = 5A$, $V_C(0^-) = 10V$, $i(t) = 10u(t)$. Determine $V_C(t)$ for $t > 0$.



Que-8→ In the circuit shown in figure, the switch 'S' is moved from position 1 to 2 at $t=0$; a steady state ~~has~~ having previously been established at position 1. Solve for current $i(t)$.

